

Controller side — full wiring (two joysticks)

Arduino Uno R4 Minima · 2× KY-023 joysticks · HC-05 master

