

HC-05 RX voltage divider

Drops the Arduino's 5 V TX signal to ≈ 3.3 V before it reaches the HC-05 RX

$$V_{\text{out}} = 5 \text{ V} \times R_2 / (R_1 + R_2) = 5 \times 2/3 \approx 3.33 \text{ V}$$

